

## OFFSET IDEAL MODEL

Diode circuits can often be analyzed using linear models.

The offset ideal model approximates the nonlinear I-V characteristic in Fig. 3 as a piecewise linear graph with a threshold voltage parameter  $V_{on}$ . The typical value for a silicon diode is  $V_{on} = 0.7$  V.

Figure 4

 


Fig. 4: Offset ideal model I-V characteristic of a diode. If  $V_D < V_{on}$ , we approximate  $I_D = 0$ . Otherwise, if  $I_D > 0$ , we approximate  $V_D = V_{on}$ . These two regions define two diode states, called OFF and ON.

Within each diode state, the diode can be replaced with a simpler linear element. If the diode is OFF, it can be replaced by an open circuit which has  $I_D = 0$  and can have any value of  $V_D$ . Otherwise, the diode is ON and it can be replaced by an element with fixed voltage drop  $V_D = V_{on}$  and any value of  $I_D$ .

Condition	State	Behavior	Replacement Rule
$V_D < V_{on}$	OFF	$I_D = 0$	
$I_D > 0$	ON	$V_D = V_{on}$	

Table 1: Diode states and replacement rules.

Figure 7

 


Fig. 7: Diode clipper with the diode OFF. When  $V_{in} < V_1 + V_{on}$  in Fig. 1, the diode is OFF and is replaced by an open circuit in this figure. Now, we apply KVL to obtain:  $V_{in} = I_1 R_1 + V_{out}$ . Note that  $I_1 = 0$  since  $R_1$  is not part of a complete circuit. Therefore,  $V_{out} = V_{in}$ .

Figure 8

 


Fig. 8: Diode clipper with the diode ON. When  $V_{in} > V_1 + V_{on}$  in Fig. 1, the diode is ON and is replaced by an element with voltage drop  $V_{on}$  in this figure. Now, we apply KVL to obtain:  $V_1 + V_{on} = V_{out}$ . Therefore,  $V_{out} = V_1 + V_{on}$ .

Combining the results from Fig. 7 and Fig. 8 gives

$$V_{out} = \begin{cases} V_{in}, & \text{if } V_{in} < V_1 + V_{on}, \\ V_1 + V_{on}, & \text{if } V_{in} > V_1 + V_{on}. \end{cases}$$

Figure 4

 


Fig. 4: Amplifier input-output characteristic.  $V_{out}$  is constant at  $V_{CC}$  in the OFF mode, linearly decreasing in the ACTIVE mode and constant at  $V_{CE,sat}$  in the SATURATED mode. The transition from OFF to ACTIVE happens at  $V_{in} = V_{BE,on}$  and the transition from ACTIVE to SATURATED happens at  $V_{in} = V_{in}^*$ , derived as (2) below.

The fact that a diode allows current to flow in only one direction means that it can rectify a sinusoidal voltage waveform by blocking its negative part.

Figure 2

 


Fig. 2: Half-wave rectifier. A half-wave rectifier circuit consists of a diode in series with a resistor. The input voltage  $V_{in}$  is applied across the diode and the resistor. The output voltage  $V_{out}$  is taken across the resistor.

Figure 4

 


Fig. 4: Half-wave rectifier with the diode ON. When  $V_{in} > V_{on}$  in Fig. 1, the diode is ON and is replaced by an element with voltage drop  $V_{on}$  in this figure. Now, we apply KVL to obtain:  $V_{in} = V_{on} + V_{out}$ . Therefore,  $V_{out} = V_{in} - V_{on}$ .

Combining the results from Fig. 3 and Fig. 4 gives

$$V_{out} = \begin{cases} 0, & \text{if } V_{in} < V_{on}, \\ V_{in} - V_{on}, & \text{if } V_{in} > V_{on}. \end{cases} \quad (1)$$

We take the following as given: the input voltage  $V_{in}$ ; the circuit constants  $V_{CC}$ ,  $R_1$  and  $R_2$ ; and the BJT parameters  $\beta$ ,  $V_{BE,on}$  and  $V_{CE,sat}$ . We now show how equations (1) to (7) define three operating modes for the BJT, called OFF, ACTIVE and SATURATED, and derive expressions for  $V_{BE}$ ,  $I_B$ ,  $I_C$  and  $V_{CE}$  in each mode.

Conditions	Mode	Behavior: Derivation and Reasons
$V_{in} < V_{BE,on}$	OFF	$V_{BE} = V_{in}$ from BJT input model (3) $I_B = 0$ from BJT input model (3) $I_C = 0$ from BJT output model (5) $V_{CE} = V_{CC}$ from output loop KVL (2)
$V_{in} > V_{BE,on}$ $V_{CE} > V_{CE,sat}$	ACTIVE	$V_{BE} = V_{BE,on}$ from BJT input model (4) $I_B = \frac{V_{in} - V_{BE,on}}{R_1}$ from input loop KVL (1) $I_C = \beta I_B$ from BJT output model (6) $V_{CE} = V_{CC} - I_C R_2$ from output loop KVL (2)
$V_{in} > V_{BE,on}$ $V_{CE} \leq V_{CE,sat}$	SATURATED	$V_{CE} = V_{CE,sat}$ from BJT output model (7) $I_C = \frac{V_{CC} - V_{CE,sat}}{R_2} \equiv I_{C,sat}$ from output loop KVL (2) $V_{BE} = V_{BE,on}$ from BJT input model (4) $I_B = \frac{V_{in} - V_{BE,on}}{R_1}$ from input loop KVL (1)

Table 1: BJT operating modes.

Note that  $I_{C,sat}$ , which is called the saturation current, is the maximum value of  $I_C$  among all the modes. In contrast,  $V_{CE,sat}$  is the minimum value of  $V_{CE}$ . After some practice, you are expected to recall and evaluate the derivation for each mode by looking at a circuit diagram like Fig. 1 or Fig. 3.

$$G = \frac{V_{CE,sat} - V_{CC}}{V_{in}^* - V_{BE,on}} \quad (1)$$

(2) The constant output voltages  $V_{CC}$  in OFF mode and  $V_{CE,sat}$  in SATURATED mode are explained by the behavior of  $V_{CE}$  in those modes. The transition input voltage  $V_{BE,on}$  between OFF and ACTIVE is the boundary between the conditions on  $V_{in}$  in those modes.

At the transition input voltage between ACTIVE and SATURATED, the BJT obeys the behavior of both of these modes. In particular, we follow these steps to derive  $V_{in}^*$ :

$$\begin{aligned} I_C &= I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_2} && \text{SATURATED mode } I_C \text{ formula} \\ I_B &= \frac{I_C}{\beta} && \text{from ACTIVE mode } I_C \text{ formula} \\ V_{in}^* &= V_{in} = V_{BE,on} + I_B R_1 && \text{from ACTIVE mode } I_B \text{ formula} \end{aligned}$$

The overall expression is:

$$V_{in}^* = V_{BE,on} + \frac{R_1}{\beta R_2} (V_{CC} - V_{CE,sat}), \quad (2)$$

where  $V_{CC}$ ,  $R_1$  and  $R_2$  are known circuit constants and  $\beta$ ,  $V_{BE,on}$  and  $V_{CE,sat}$  are known BJT parameters. Substituting equation (2) into equation (1), gives another formula for the gain of the common emitter amplifier:

$$G = -\frac{\beta R_2}{R_1} \quad (3)$$

Figure 5

 


Fig. 5: Voltage signal amplification. If  $V_{in}$  is a signal between  $V_{BE,on}$  and  $V_{in}^*$ , then  $V_{out}$  is an amplified and inverted copy that exists between  $V_{CC}$  and  $V_{CE,sat}$ .

Figure 6

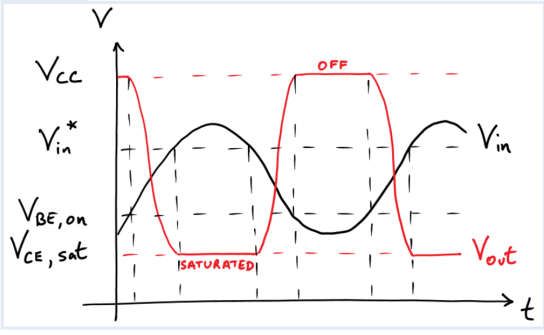


Fig. 6: Voltage signal amplification with clipping. If  $V_{in}$  is a signal that goes below  $V_{BE,on}$  and above  $V_{in}^*$ , then  $V_{out}$  is an amplified and inverted copy that is clipped at  $V_{CC}$  above and  $V_{CE,sat}$  below.

Conditions	Mode	Behavior under Linear Model
$V_{GS} < V_{TH}$	OFF	$I_D = 0$
$V_{GS} > V_{TH}$ $V_{DS} > V_{GS} - V_{TH}$	ACTIVE	$I_D = k(V_{GS} - V_{TH})^2$
$V_{GS} > V_{TH}$ $V_{DS} < V_{GS} - V_{TH}$	OHMIC	$I_D = k(V_{GS} - V_{TH})V_{DS}$

Table 1: NMOS transistor operating modes.

Figure 9

 


Fig. 9: NMOS transistor connected to a Thévenin subcircuit. You can apply the load line method to analyze an NMOS transistor connected to a Thévenin subcircuit, consisting of  $V_{DD}$  and  $R_D$ . Intersect the NMOS output I-V characteristic in Fig. 8 with the Thévenin subcircuit's I-V characteristic to find the operating point ( $V_{DS}$ ,  $I_D$ ) and the mode which it represents.

Figure 7

 


Fig. 7: The circuit symbol for an NMOS transistor. The input voltage  $V_{GS}$  drops from gate to source. (Note that  $V_{GS} = V_G$  in Fig. 3 and Fig. 4 since the body and source terminals are grounded in those diagrams.) On the output side,  $I_D$  flows into the drain and  $V_{DS}$  drops from drain to source. Notice that the NMOS transistor symbol incorporates the symbol for a capacitor to signify the gate's capacitive properties.

If the input  $V_{GS}$  is fixed, an output I-V characteristic can be traced relating  $I_D$  to  $V_{DS}$ . Varying  $V_{GS}$  therefore produces a family of curves. We model the operation of an NMOS transistor by dividing the I-V space into 3 modes, OFF, ACTIVE and OHMIC, and fitting linear equations to each I-V curve in each mode.

MOSFET Type	Logic Circuit Symbol	$A = 0$ Approximation	$A = 1$ Approximation
NMOS			
PMOS			

Table 1: MOSFET logic circuit symbols and approximations.

The logic circuit symbol for an NMOS transistor (shown above in Table 1) is slightly different to its analog circuit symbol. In a logic circuit, an NMOS transistor is always drawn with the drain terminal at the top and the source terminal at the bottom. In contrast, the logic circuit symbol for a PMOS transistor is always drawn with the source terminal at the top and the drain terminal at the bottom. The PMOS transistor symbol includes a bubble at the gate terminal that represents logical inversion (to be explained below). Note also that the input  $A$  labeled at the gate terminal of each MOSFET in Table 1 is a logical value. When  $A = 0$ , the voltage at the gate terminal is close to ground; when  $A = 1$ , the gate terminal voltage is close to  $V_{DD}$ .

Recall that the energy stored by a capacitor is  $0.5CV^2$ . Thus, each time a MOSFET's output goes from 0 to 1 and back to 0, the load capacitance charges and discharges with  $0.5CV_{DD}^2$  J of energy. An additional  $0.5CV_{DD}^2$  J is wasted during each cycle due to inefficient charging. Charging a capacitor efficiently requires the applied voltage to be increased gradually, but this would be too slow for high-performance electronics. Therefore, a MOSFET consumes a total of  $CV_{DD}^2$  J of energy every time its output completes a full cycle. If the MOSFET switches at a rate of  $f$  Hz (i.e. cycles per second), then its power consumption is  $fCV_{DD}^2$  W. We now extend this analysis to an entire chip. Suppose the chip contains  $n$  MOSFETs but only a proportion  $\alpha$  of them are actively switching output at any time on average. Then the average number of switching MOSFETs on the chip is  $\alpha n$ , where the proportion  $\alpha$  is known as the activity factor. Finally, if  $C$  is the MOSFET's average load capacitance and  $f$  is the cycling frequency of the chip, the power consumption of the chip is:

$$P = \alpha n f C V_{DD}^2$$